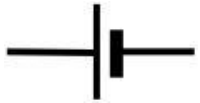


Match the symbol to the correct name and use.



cell

motor

closed switch

battery

buzzer

open switch

bulb

Transfers chemical energy to electrical energy.

Two cells in series.

Transfers electrical energy to sound energy.


Transfers electrical energy to movement.

Completes the circuit.

Transfers electrical energy to light energy.

Breaks the circuit.

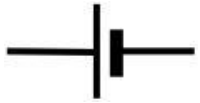Match the symbol to the correct name and use.



cell

motor

closed switch

battery

buzzer

open switch

bulb

Transfers chemical energy  
to electrical energy.

Two cells in series.

Transfers electrical energy  
to sound energy.

Transfers electrical energy  
to movement.

Completes the circuit.

Transfers electrical energy  
to light energy.

Breaks the circuit.