

Draw these circuits scientifically using the correct symbols



